

ZXSC310 Solution for a 1W High Power White LED

Aim

This design note shows the ZXSC310 driving a 1W LED. The LED has 180Cd light output from a forward current of 350mA. The solution is optimised to drive the 1W LED at 350mA DC current from a dual cell input.

Circuit diagram

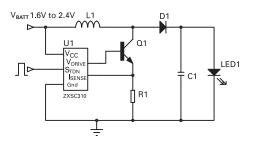

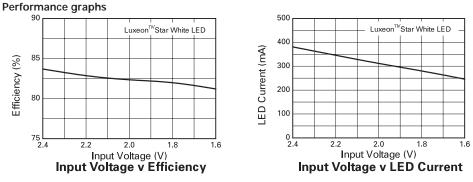

Bill of Materials

Reference	Part No.	Value	Manufacturer	Contact Details
U1	ZXSC310E5	LED driver	Zetex	www.zetex.com
Q1	FMMT617	3A, Iow V _{CE(SAT)}	Zetex	www.zetex.com
D1	ZHCS1000	2A, low V _F	Zetex	www.zetex.com
L1	DO3316P-223	22uH, 2A	Coilcraft	www.coilcraft.com
R1	Generic	22mΩ	Generic	
C1	Generic	2.2μF	Generic	
LED1	LXHL-NW98	White LED	Lumileds	www.lumileds.com

ISSUE 3 - MARCH 2004



DN61 - 1

Design Note 61 ISSUE 3 - MARCH 2004

© Zetex plc 2004

Europe	Americas	Asia Pacific	Corporate Headquaters
Zetex GmbH	Zetex Inc	Zetex (Asia) Ltd	Zetex plc
Streitfeldstraße 19	700 Veterans Memorial Hwy	3701-04 Metroplaza Tower 1	Fields New Road, Chadderton
D-81673 München	Hauppauge, NY 11788	Hing Fong Road, Kwai Fong	Oldham, OL9 8NP
Germany	USA	Hong Kong	United Kingdom
Telefon: (49) 89 45 49 49 0	Telephone: (1) 631 360 2222	Telephone: (852) 26100 611	Telephone (44) 161 622 4444
Fax: (49) 89 45 49 49 49	Fax: (1) 631 360 8222	Fax: (852) 24250 494	Fax: (44) 161 622 4446
europe.sales@zetex.com	usa.sales@zetex.com	asia.sales@zetex.com	hq@zetex.com

This publication is issued to provide outline information only which (unless agreed by the Company in writing) may not be used, applied or reproduced for any purpose or form part of any order or contract or be regarded as a representation relating to the products or services concerned. The Company reserves the right to alter without notice the specification, design, price or conditions of supply of any product or service.

